

THE AMERICAN  
UNIVERSITY IN CAIRO  
الجامعة الأمريكية بالقاهرة

# CSCE 3301: COMPUTER ARCHITECTURE

Lecture 6: RISC-V Single Cycle Implementation (Continued)

Dr. Cherif Salama

Copyright notice: Some of these slides and figures are either reproduced or adapted from the references mentioned at end of the presentation


# BUILDING A DATAPATH

- Datapath
  - Elements that process data and addresses in the CPU
    - Registers, ALUs, mux's, memories, ...
- We will build a RISC-V datapath incrementally
  - Refining the overview design






# INSTRUCTION FETCH

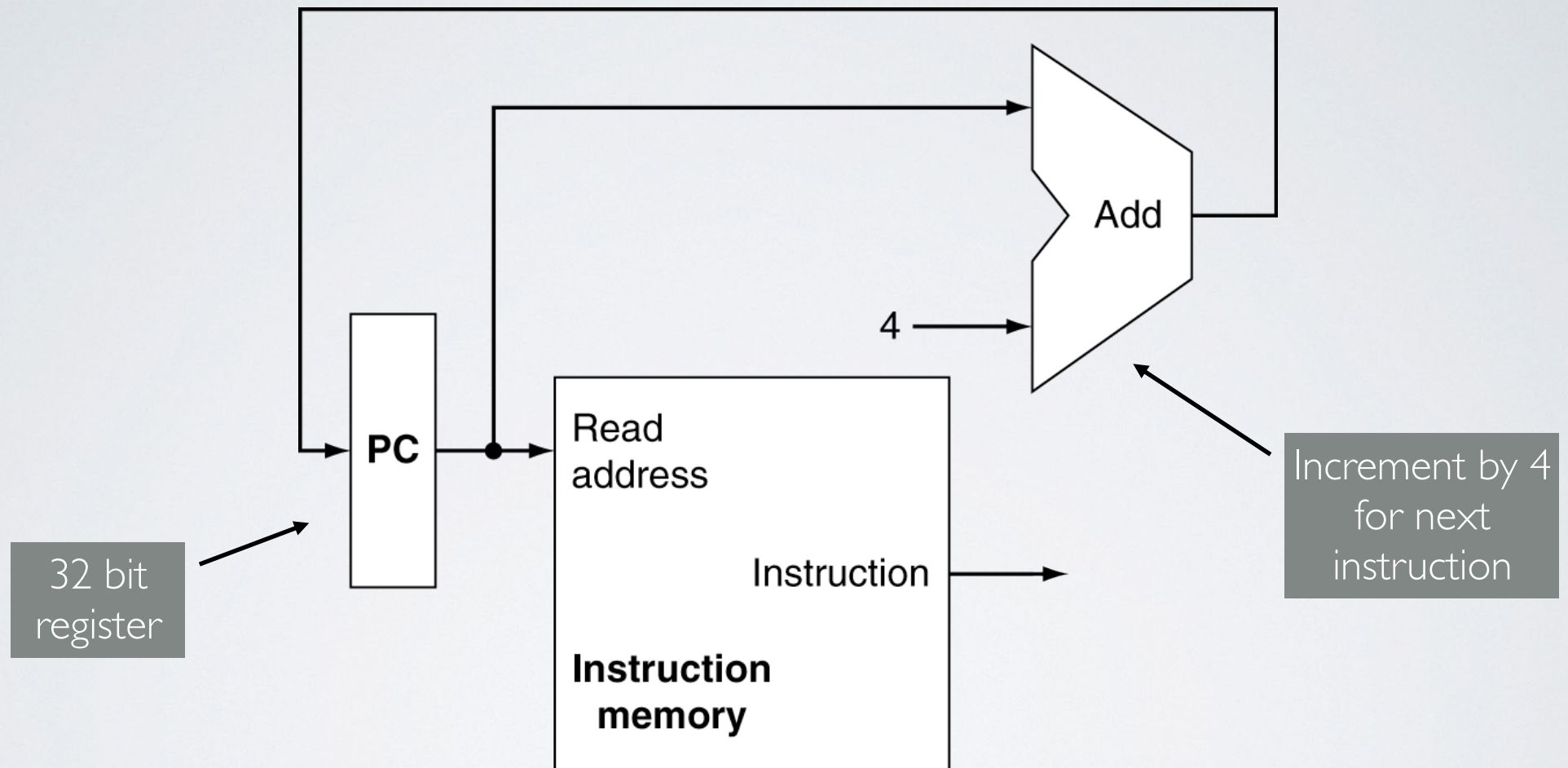

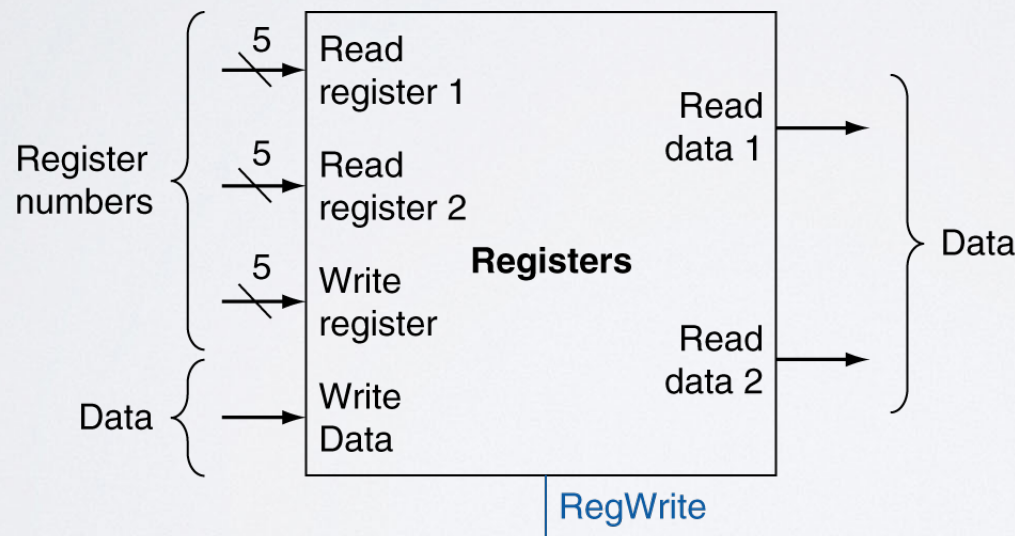
# R-FORMAT INSTRUCTIONS

- Read two register operands
- Perform arithmetic/logical operation
- Write register result



a. Registers

 


b. ALU



 
# LOAD/STORE INSTRUCTIONS

- Read register operands
- Calculate address using 12-bit offset
  - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory



a. Data memory unit

 

b. Immediate generation unit






# BRANCH INSTRUCTIONS

- Read register operands
- Compare operands
  - Use ALU, subtract and check Zero output
- Calculate target address
  - Sign-extend displacement
  - Shift left 1 place (halfword displacement)
  - Add to PC value



# BRANCH INSTRUCTIONS

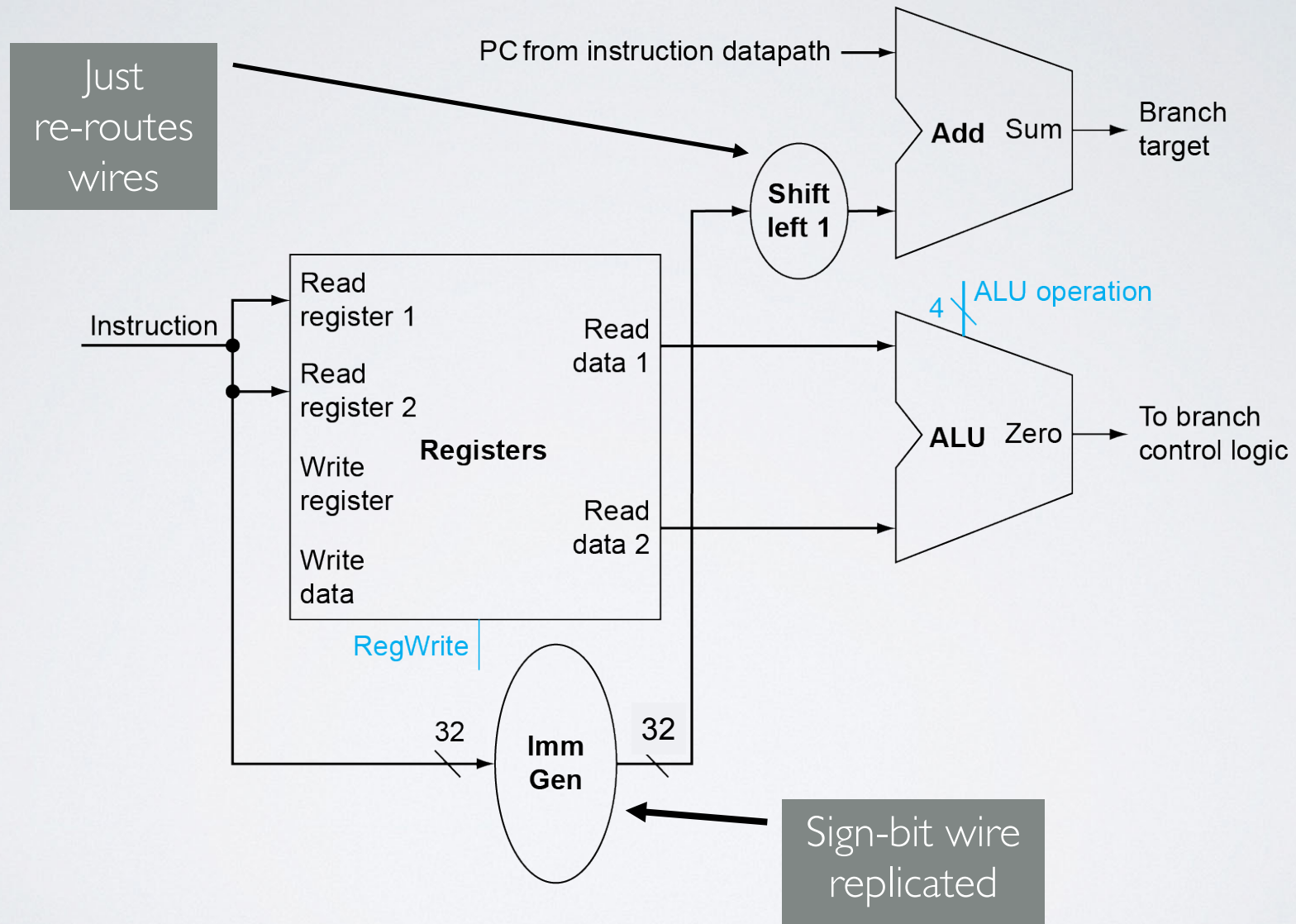


# COMPOSING THE ELEMENTS

- First-cut data path does an instruction in one clock cycle
  - Each datapath element can only do one function at a time
  - Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions






# R-TYPE/LOAD/STORE DATAPATH

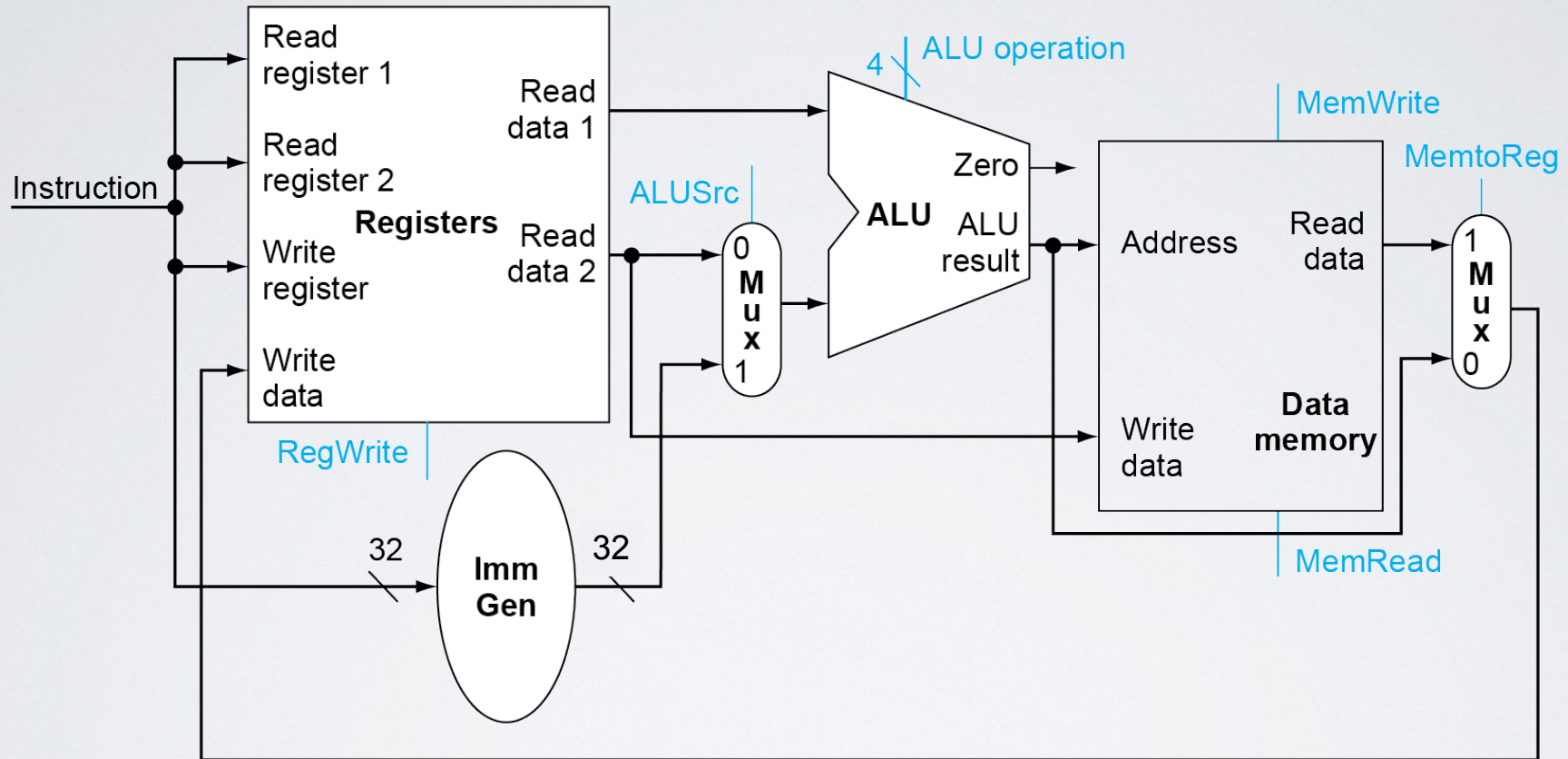

# FULL DATAPATH

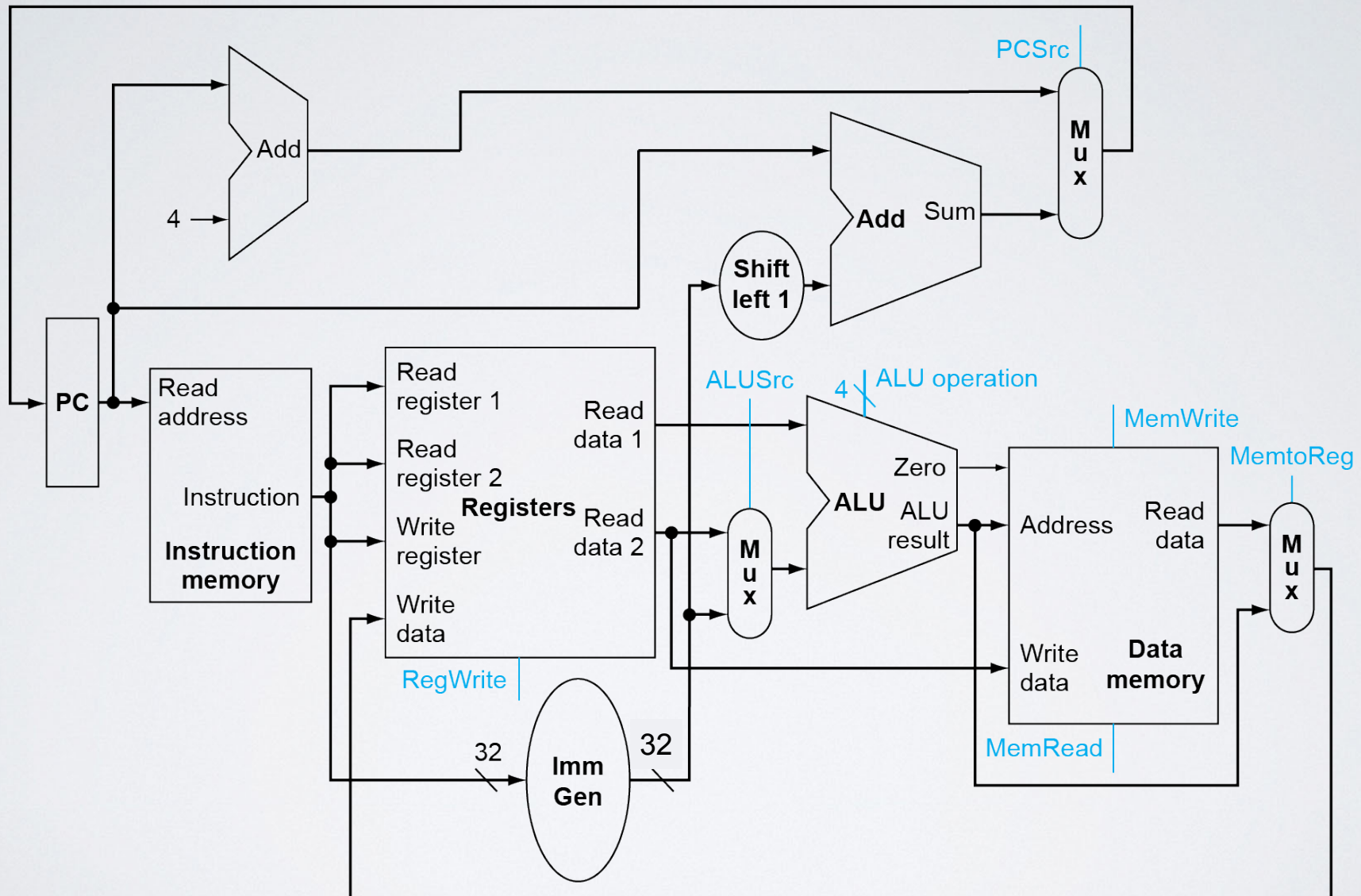

# ALU CONTROL

- ALU used for
  - Load/Store: Function = add
  - Branch: Function = subtract
  - R-type: Function depends on opcode

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract





# ALU CONTROL

- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control

opcode	ALUOp	Operation	funct7	funct3	ALU function	ALU control
lw	00	load word	XXXXXXXX	XXX	add	0010
sw	00	store word	XXXXXXXX	XXX	add	0010
beq	01	branch equal	XXXXXXXX	XXX	subtract	0110
R-type	10	add	0000000	000	add	0010
		subtract	0100000	000	subtract	0110
		AND	0000000	111	AND	0000
		OR	0000000	110	OR	0001



# THE MAIN CONTROL UNIT


- Control signals derived from instruction

Name (Bit position)	Fields					
	31:25	24:20	19:15	14:12	11:7	6:0
(a) R-type	funct7	rs2	rs1	funct3	rd	opcode
(b) I-type	immediate[11:0]		rs1	funct3	rd	opcode
(c) S-type	immed[11:5]	rs2	rs1	funct3	immed[4:0]	opcode
(d) SB-type	immed[12,10:5]	rs2	rs1	funct3	immed[4:1,11]	opcode

ALUOp		Funct7 field						Funct3 field				Operation
ALUOp1	ALUOp0	I[31]	I[30]	I[29]	I[28]	I[27]	I[26]	I[25]	I[14]	I[13]	I[12]	
0	0	X	X	X	X	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	X	X	X	X	0110
1	X	0	0	0	0	0	0	0	0	0	0	0010
1	X	0	1	0	0	0	0	0	0	0	0	0110
1	X	0	0	0	0	0	0	0	1	1	1	0000
1	X	0	0	0	0	0	0	0	1	1	0	0001




# DATAPATH WITH CONTROL

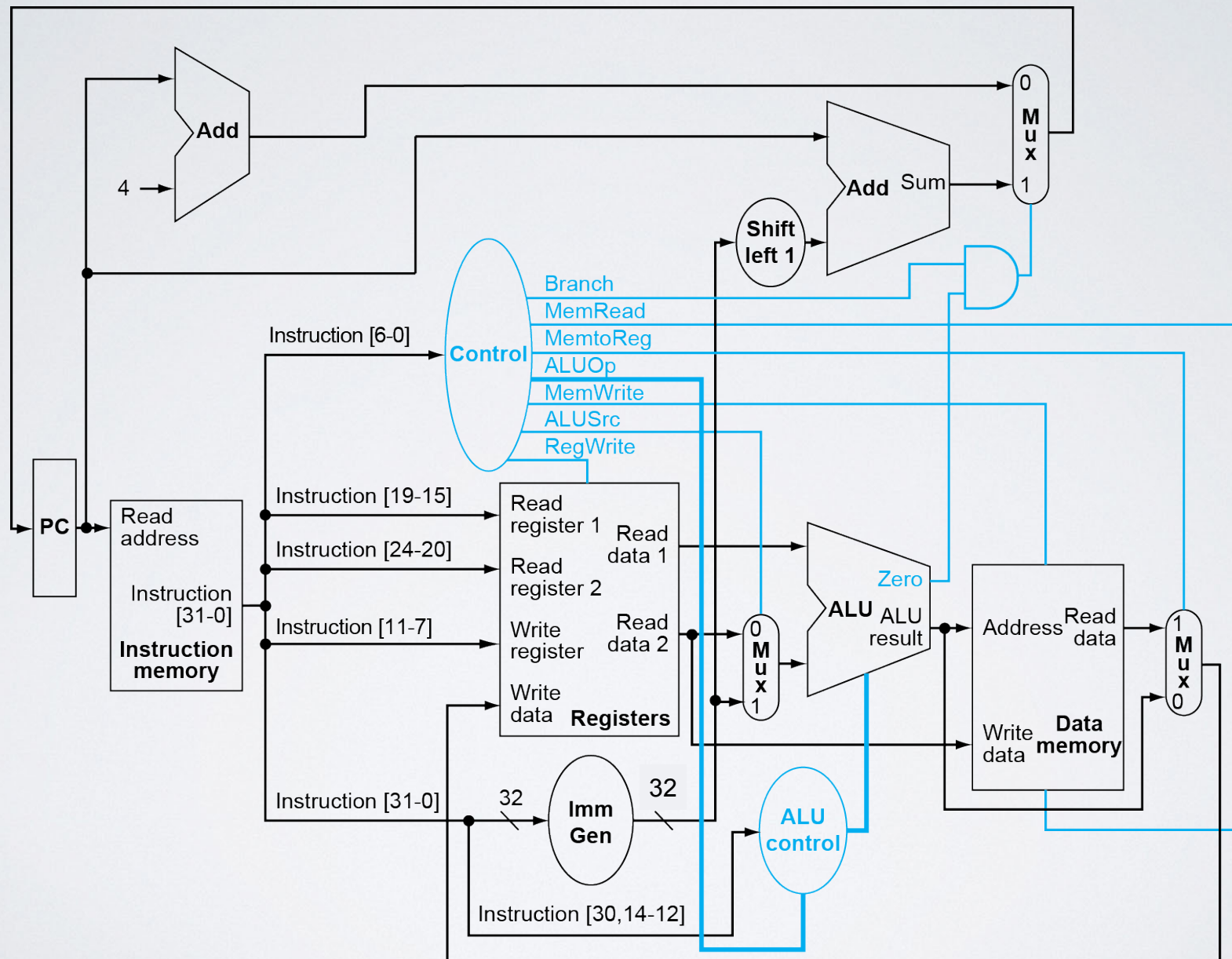





# R-TYPE INSTRUCTION

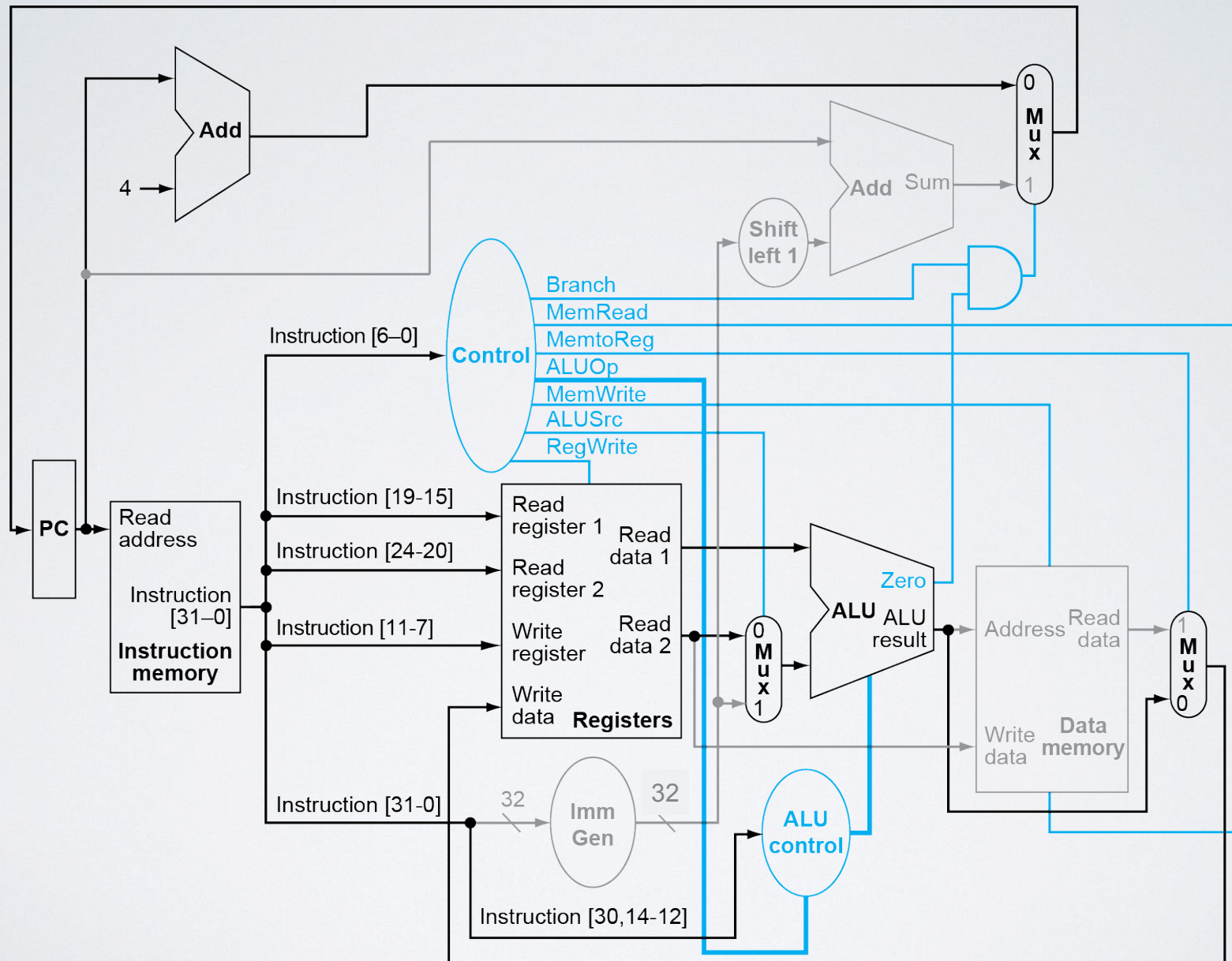

# LOAD INSTRUCTION

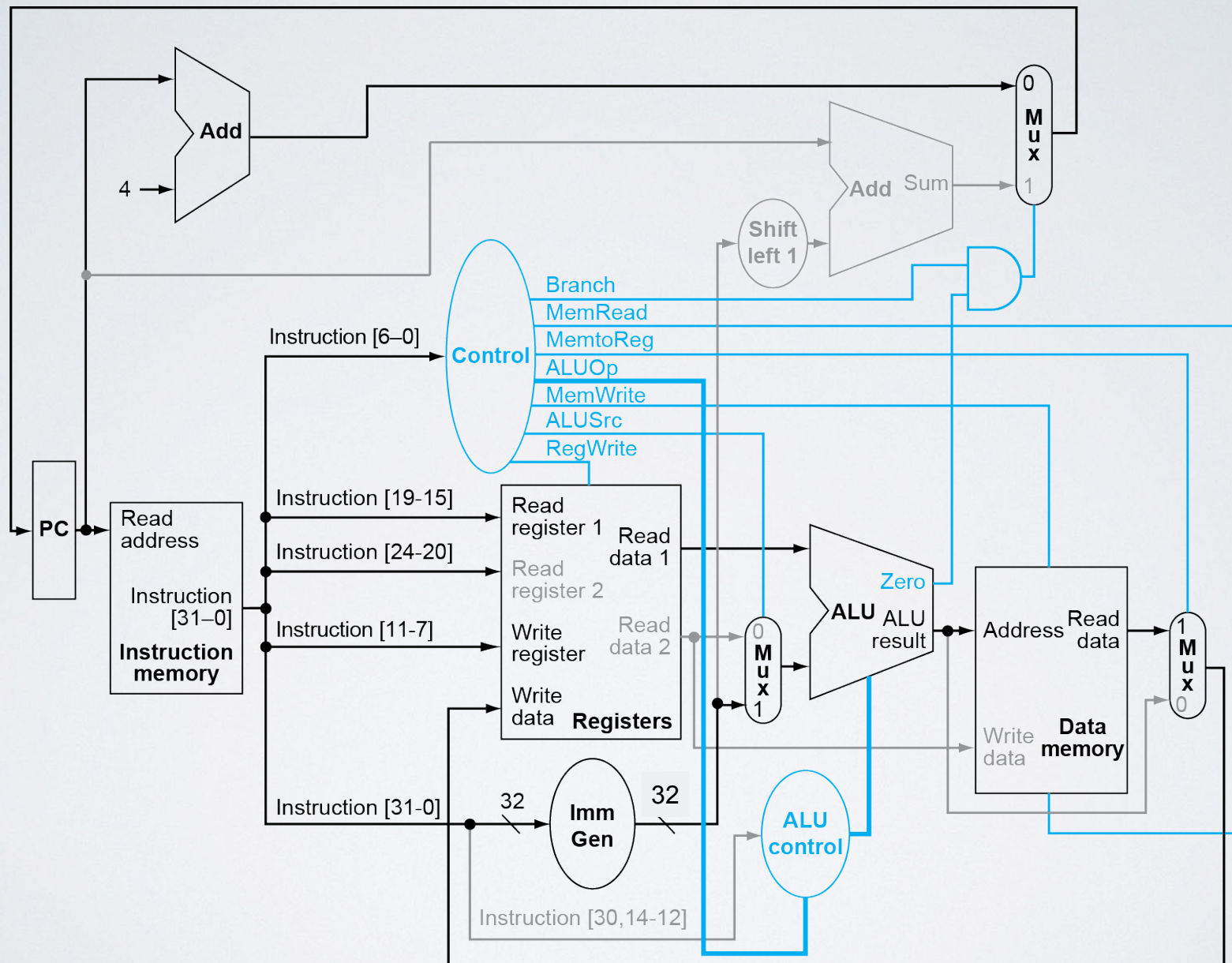

# BEQ INSTRUCTION

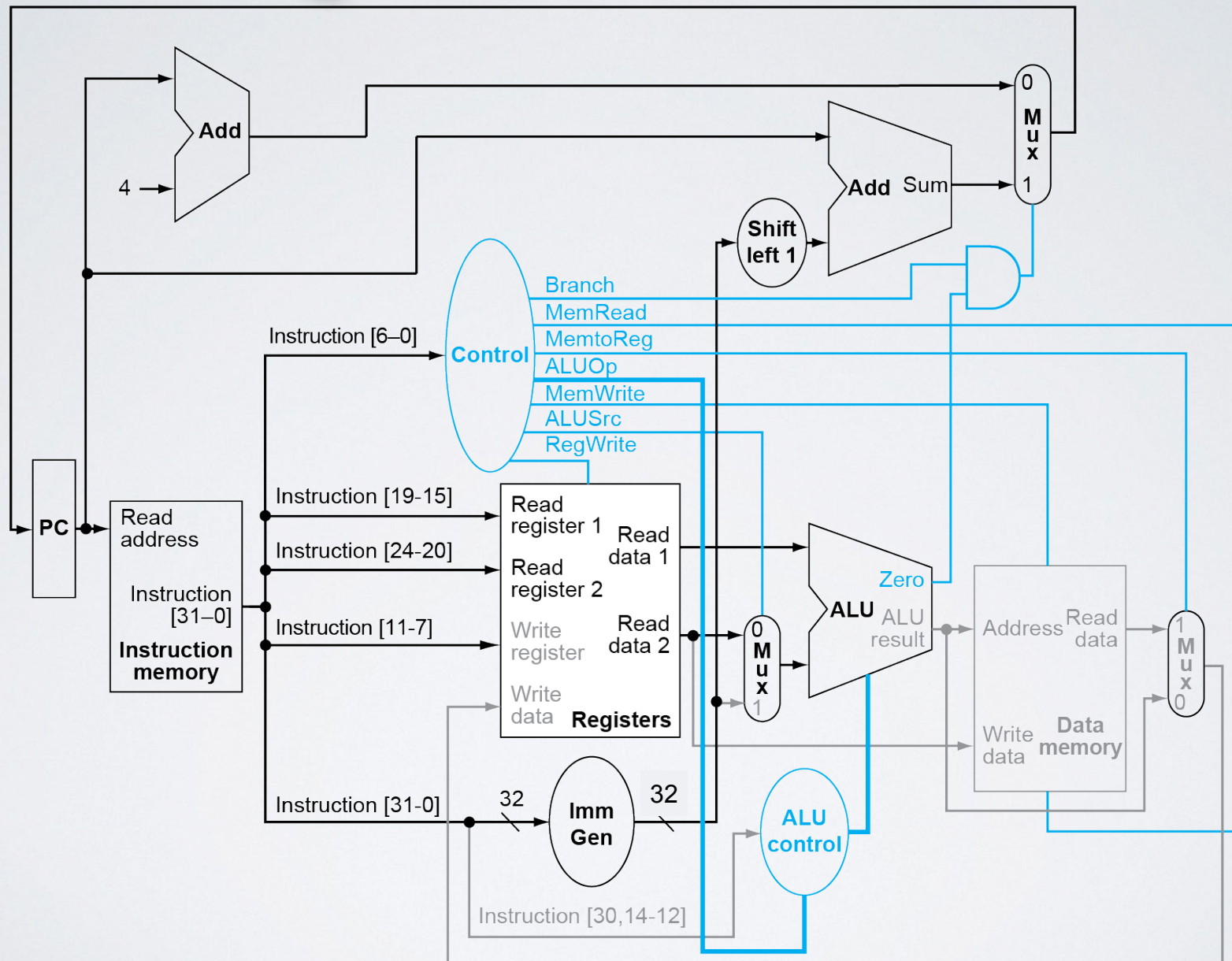



# PERFORMANCE ISSUES

- Longest delay determines clock period
  - Critical path: load instruction
  - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period for different instructions
- Violates design principle
  - Making the common case fast
- We will improve performance by pipelining



# REFERENCES

- David Patterson and John L. Hennessy, *Computer Organization and Design: RISC-V Edition*, Morgan Kaufmann, 2017

